

# Binary Multiplier and Magnitude Comparator


Sparsh Mittal

# 2-bit multiplier

- The first partial product is formed by multiplying  $B_1B_0$  by  $A_0$ .
- Multiplication of two bits such as  $A_0$  and  $B_0$  produces a 1 if both bits are 1; otherwise, it produces a 0. → An AND operation.
- The second partial product is formed by multiplying  $B_1B_0$  by  $A_1$  and shifting one position to the left.
- The two partial products are added with two half-adder (HA) circuits.

|       |          |          |       |
|-------|----------|----------|-------|
|       | $B_1$    | $B_0$    |       |
|       | $A_1$    | $A_0$    |       |
|       | <hr/>    |          |       |
|       | $A_0B_1$ | $A_0B_0$ |       |
|       |          |          |       |
|       | $A_1B_1$ | $A_1B_0$ |       |
|       | <hr/>    |          |       |
| $C_3$ | $C_2$    | $C_1$    | $C_0$ |

# Logic diagram

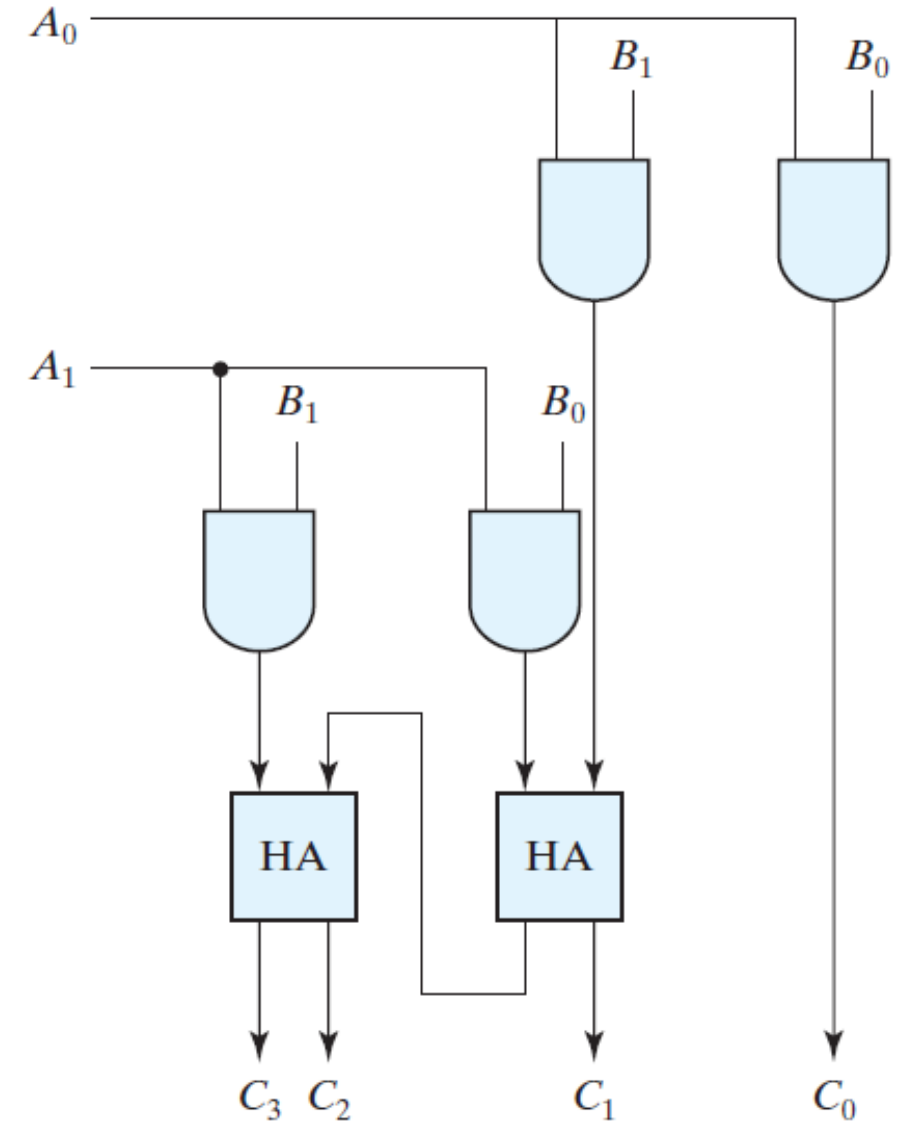


# Multiplication of $>2$ bits

- A bit of the multiplier is ANDed with each bit of multiplicand in as many levels as there are bits in the multiplier.
- The binary output in each level of AND gates is added with partial product of the previous level to form a new partial product.
- The last level produces the product.
- For  $J$  multiplier bits and  $K$  multiplicand bits, we need  $(J * K)$  AND gates and  $(J - 1) K$ -bit adders to produce a product of  $(J + K)$  bits.
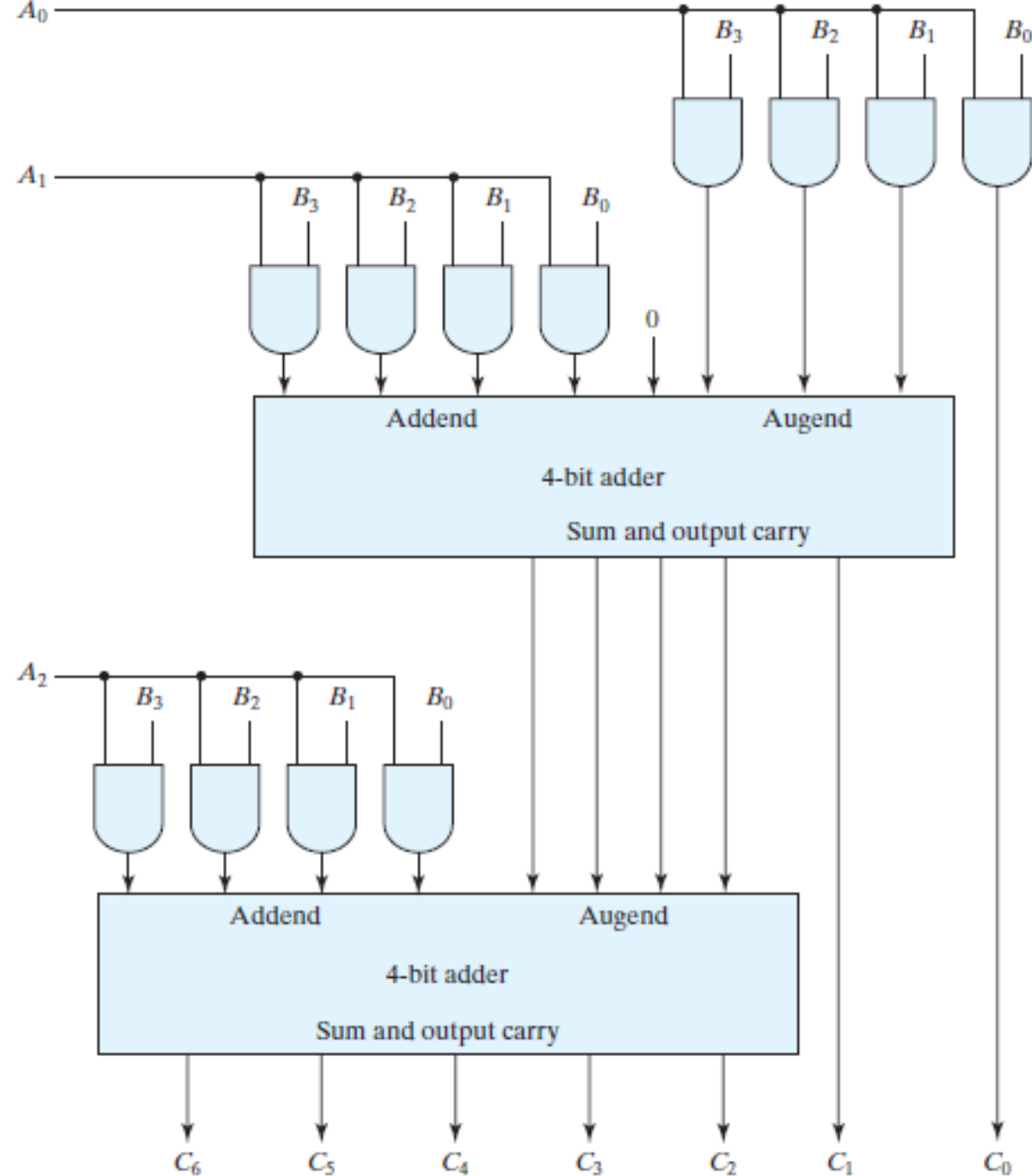
# Example: 4b\*3b multiplication

- The multiplicand  $B_3B_2B_1B_0$
- The multiplier by  $A_2A_1A_0$ .
- Since  $K = 4$  and  $J = 3$ , we need 12 AND gates and two 4-bit adders to produce a product of seven bits.





# Magnitude Comparator

# *Magnitude comparator*

- The outcome of the comparison is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$ , or  $A < B$ .
- Making a truth table is infeasible
- Given the regularity, we can design an algorithm

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

XNOR To check bitwise equality  $x_i = A_i B_i + A'_i B'_i$  for  $i = 0, 1, 2, 3$

AND of bitwise equality signals to check number equality  $(A = B) = x_3 x_2 x_1 x_0$

# Finding $A > B$ or $A < B$

- We inspect the relative magnitudes of pairs of significant digits, starting from the most significant position.
- If the two digits of a pair are equal, we compare the next lower significant pair of digits.
- The comparison continues until a pair of unequal digits is reached.
- If the corresponding digit of  $A$  is 1 and that of  $B$  is 0, we conclude that  $A > B$ .
- If the corresponding digit of  $A$  is 0 and that of  $B$  is 1, we have  $A < B$ .



# Expressions

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

- The unequal outputs can use the same gates that are needed to generate the equal output.

# Circuit

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

- This is a multilevel implementation and has a regular pattern.

