

Shifter and Rotator

Sparsh Mittal



Understanding sign/zero extension

Extension

- Extension is required when we want to preserve the numeric value, while we represent a number using more bits; or store it in a register with more number of bits.
- There are two possibilities: sign-extension and zero-extension
- Sign-extension: replicate the sign bit to the left
- Zero-extension: replicate zero bit to the left.

Understanding extension

Case 1: Assume our 8b data is 1101 0011. We need to store it in a 16b register.



Case 2: Assume our 8b data is 0101 0011. We need to store it in a 16b register.



Notice that in case 2, sign- and zero-extension have the same impact.

Sign extension example.

- Write the value of -7 in 32 bits.


$$(-7)_{10} = (1001)_2 \text{ \# 2's complement representation.}$$

- Sign extension in 32-bit representation:


$$(-7)_{10} = (1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1111\ 1001)_2$$

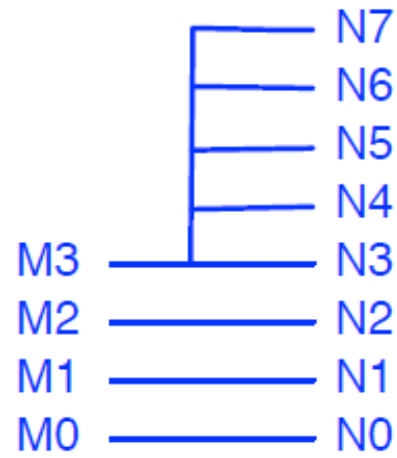Question

- Draw a circuit for a sign extension unit with a 4-bit input and an 8-bit output



Arithmetic and logical shifts

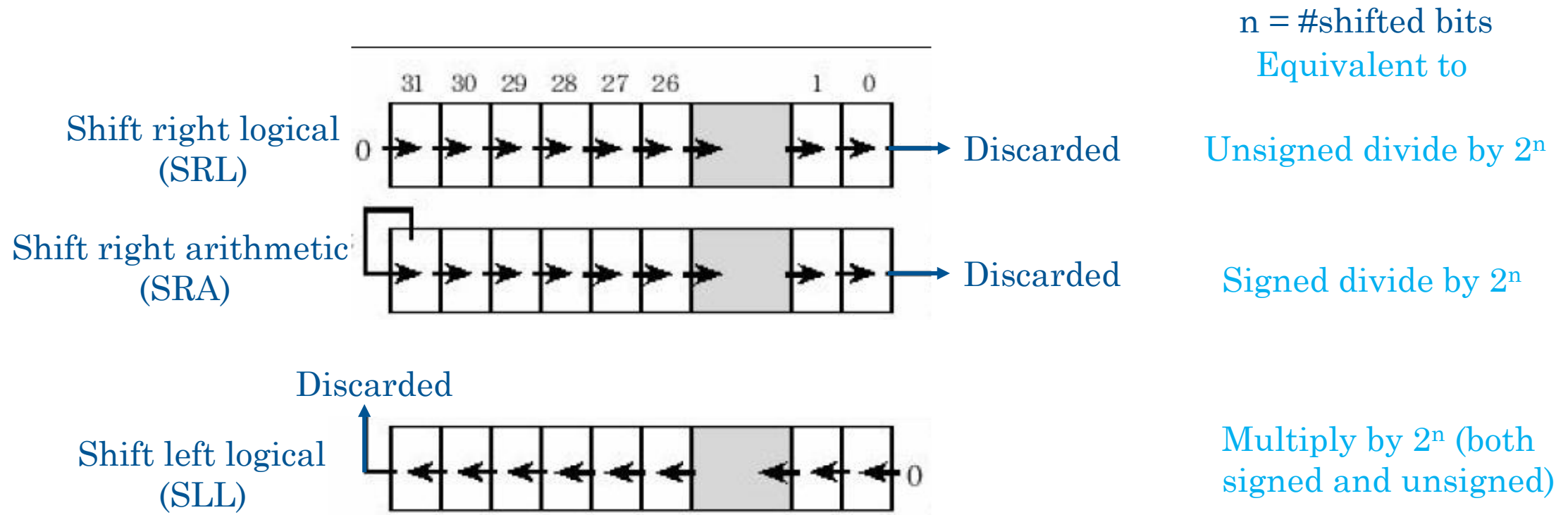

Visual explanation



a1 0x1

On doing, “**a2 = a0 sll a1**”, we are shifting a0 left by 1. So now, the value of a2 is:



On doing, “**a3 = a0 srl a1**”, we are shifting a0 right by 1. It's logical shift, so new bit filled will be 0. a3 will be



On doing, “**a4 = a0 sra a1**”, we are shifting a0 right by 1. It's arithmetic shift, so new bit filled will be the same as the sign bit, which is 1. a4 will be



- There is no shift-left arithmetic (SLA) operation. Why?
- Answer: Two's complement ensures that SLA and SLL lead to same effect.

Examples

❑ Right shift requires both logical and arithmetic modes

- Assuming 4 bits
- $(4_{10}) \gg 1 = (0100_2) \gg 1 = 0010_2 = 2_{10}$ Correct!
- $(-4_{10}) \gg_{\text{logical}} 1 = (1100_2) \gg_{\text{logical}} 1 = 0110_2 = 6_{10}$ For signed values, Wrong!
- $(-4_{10}) \gg_{\text{arithmetic}} 1 = (1100_2) \gg_{\text{arithmetic}} 1 = 1110_2 = -2_{10}$ Correct!
- Arithmetic shift replicates sign bits at MSB

❑ Left shift is the same for logical and arithmetic

- Assuming 4 bits
- $(2_{10}) \ll 1 = (0010_2) \ll 1 = 0100_2 = 4_{10}$ Correct!
- $(-2_{10}) \ll_{\text{logical}} 1 = (1110_2) \ll_{\text{logical}} 1 = 1100_2 = -4_{10}$ Correct!

Shifter

- An N -bit shifter can be built from N $N:1$ multiplexers.
- The input is shifted by 0 to $N-1$ bits, depending on the value of the $\log_2 N$ -bit select lines.

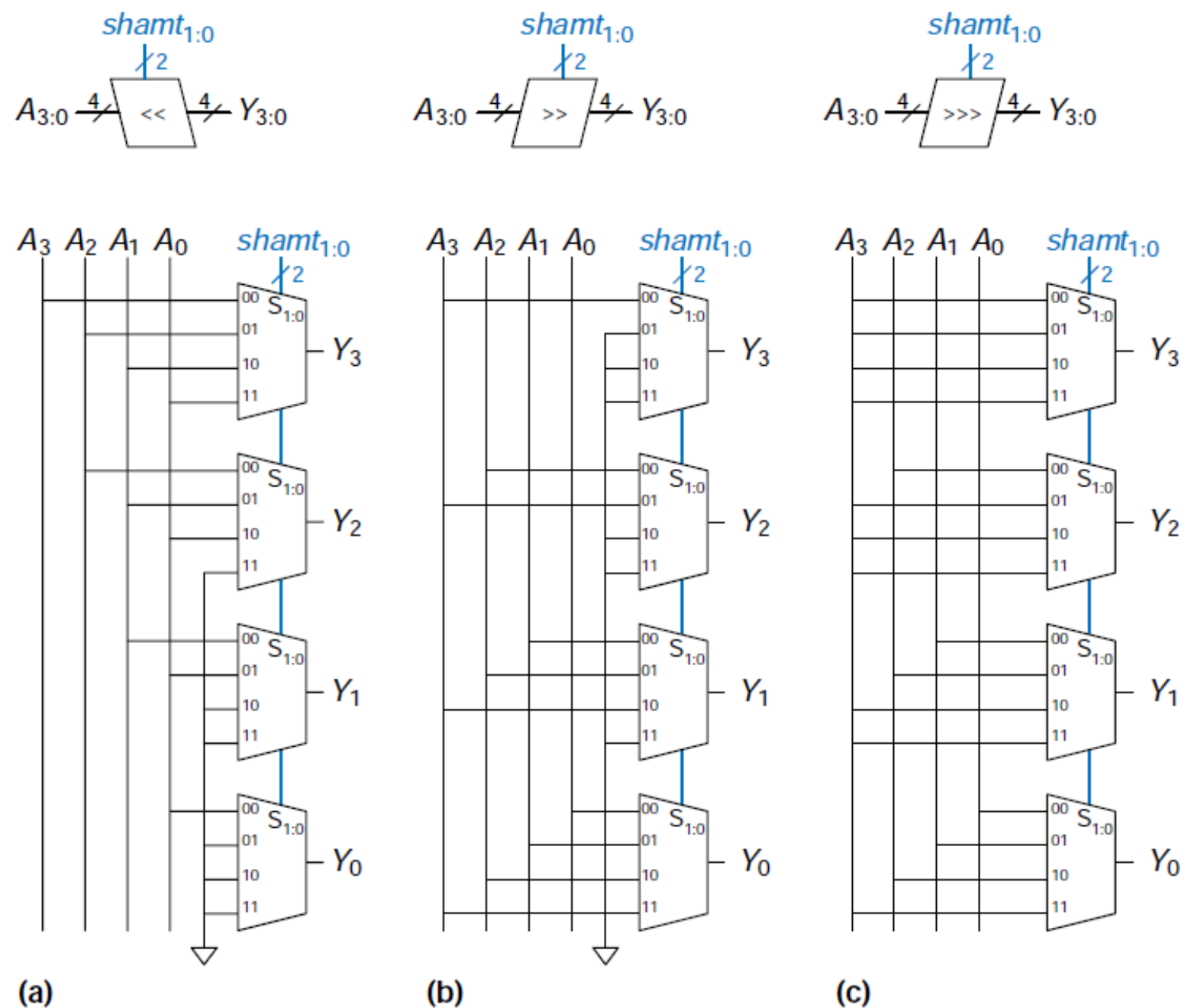


Figure 5.16 4-bit shifters: (a) shift left, (b) logical shift right, (c) arithmetic shift right

Rotator

- **Rotator**—rotates number in circle such that empty spots are filled with bits shifted off the other end.
- $11001 \text{ ROR } 2 = 01110;$
- $11001 \text{ ROL } 2 = 00111$