

JK and T Flipflop

Sparsh Mittal

Versatility of JK flipflop


A flipflop can do three operations: Set it to 1, reset it to 0, or complement its output.

But, D flipflop can do only two operations since it has only 1 input.


Synchronized by a clock signal, the JK flip-flop has two inputs and performs all three operations.

JK Flip-flop

$$D = JQ' + K'Q$$

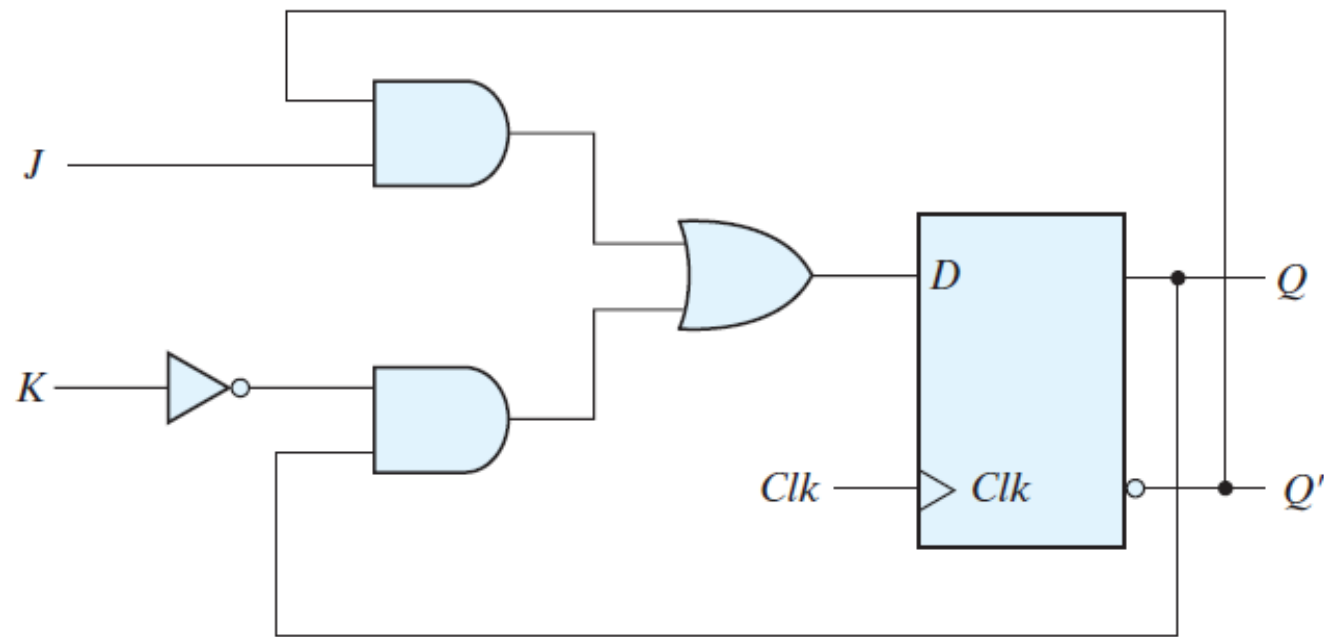

(a) Circuit diagram

 

(b) Graphic symbol

FIGURE 5.12
JK flip-flop

JK flipflop

$$D = JQ' + K'Q$$

The J input sets the flip-flop to 1, the K input resets it to 0, and when both inputs are enabled, the output is complemented.

When $J = 1$ and $K = 0$, $D = Q + Q' = 1$, so the next clock edge sets the output to 1.

When $J = 0$ and $K = 1$, $D = 0$, so the next clock edge resets the output to 0.

When both $J = K = 1$ and $D = Q'$, the next clock edge complements the output.

When both $J = K = 0$ and $D = Q$, the clock edge leaves the output unchanged.

Toggle (T) flipflop

 


FIGURE 5.13
 T flip-flop

$$D = T \oplus Q = TQ' + T'Q$$

The complementing flip-flop is useful for designing binary counters.

Characteristic table

Table 5.1
Flip-Flop Characteristic Tables

| <i>JK Flip-Flop</i> | | | |
|----------------------------|-----------------|------------------------|------------|
| <i>J</i> | <i>K</i> | <i>Q(t + 1)</i> | |
| 0 | 0 | $Q(t)$ | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | $Q'(t)$ | Complement |

| <i>D Flip-Flop</i> | | |
|---------------------------|------------------------|-------|
| <i>D</i> | <i>Q(t + 1)</i> | |
| 0 | 0 | Reset |
| 1 | 1 | Set |

| <i>T Flip-Flop</i> | | |
|---------------------------|------------------------|------------|
| <i>T</i> | <i>Q(t + 1)</i> | |
| 0 | $Q(t)$ | No change |
| 1 | $Q'(t)$ | Complement |

Characteristic Equation

$$Q(t + 1) = D$$

$Q(t)$ is simply written as Q .

$$Q(t + 1) = JQ' + K'Q$$

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

Asynchronous (direct) set/reset


Some flip-flops have asynchronous inputs to force the flip-flop to a particular state independently of the clock.

Direct set/reset: setting flip-flop to 1 or 0.


When power is turned on, the state of the flip-flops is unknown.

Direct inputs bring all flip-flops to a known starting state prior to the clocked operation.

 Positive-edge-triggered D flip-flop with active-low asynchronous reset



(a) Circuit diagram

 


(b) Graphic symbol

| R | Clk | D | Q | Q' |
|-----|------------|-----|-----|------|
| 0 | X | X | 0 | 1 |
| 1 | \uparrow | 0 | 0 | 1 |
| 1 | \uparrow | 1 | 1 | 0 |


(b) Function table

Question


The 100 kHz square wave is applied to the clock input of the flip-flops. If the Q output is initially '0', draw the Q output waveforms. Also, determine the frequency of the Q output.

 

Circuit 1

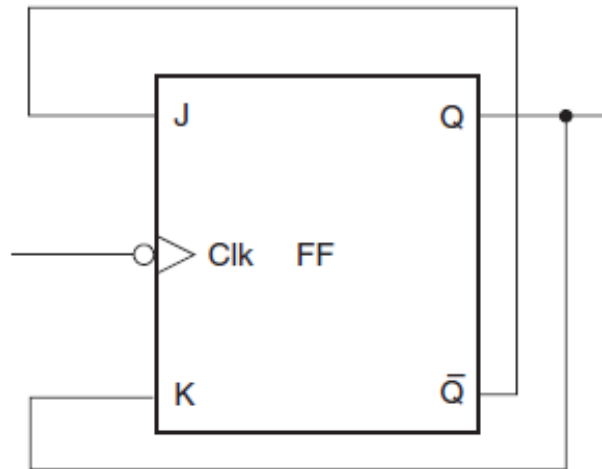

Circuit 2

 

Solution of circuit 1



Q is initially '0'. $\rightarrow J=1, K=0$.

At first negative edge of clock, Q becomes 1.


$\rightarrow J=0, K=1$

With the next negative edge, $Q=0$.

 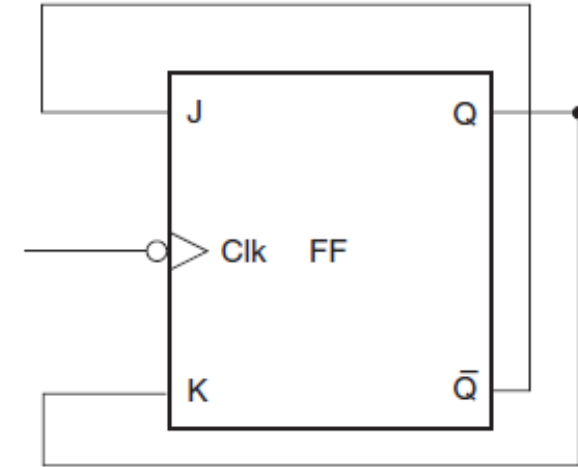This process continues, and Q alternately becomes '1' and '0'.



Input

 



Output

Solution of circuit 2


The circuit behaves similarly to first circuit.

Only change: transition happens on positive edge.

  In both cases, output frequency is half of input frequency.





Input

 

Output

  Question


The 100 kHz square waveform is applied to the clock input of T flip-flop. If the Q output is initially '0', draw the Q output waveforms. Also, determine the frequency of the Q output.



Solution

The circuit acts as a frequency divider.

Transition happens on positive edge.

 

The Big Picture: Storage Elements

- Latches and Flip-Flops
 - Very fast, parallel access
 - Very expensive (one bit costs tens of transistors)
- Static RAM (SRAM)
 - Relatively fast
 - Expensive (one bit costs 6+ transistors)
- Dynamic RAM (DRAM)
 - Slower, reading destroys content (refresh), needs special process for manufacturing
 - Cheap (one bit costs only one transistor plus one capacitor)
- Other storage technology (flash memory, hard disk, tape)
 - Much slower, access takes a long time,