

# Multiplexer


Sparsh Mittal




- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.
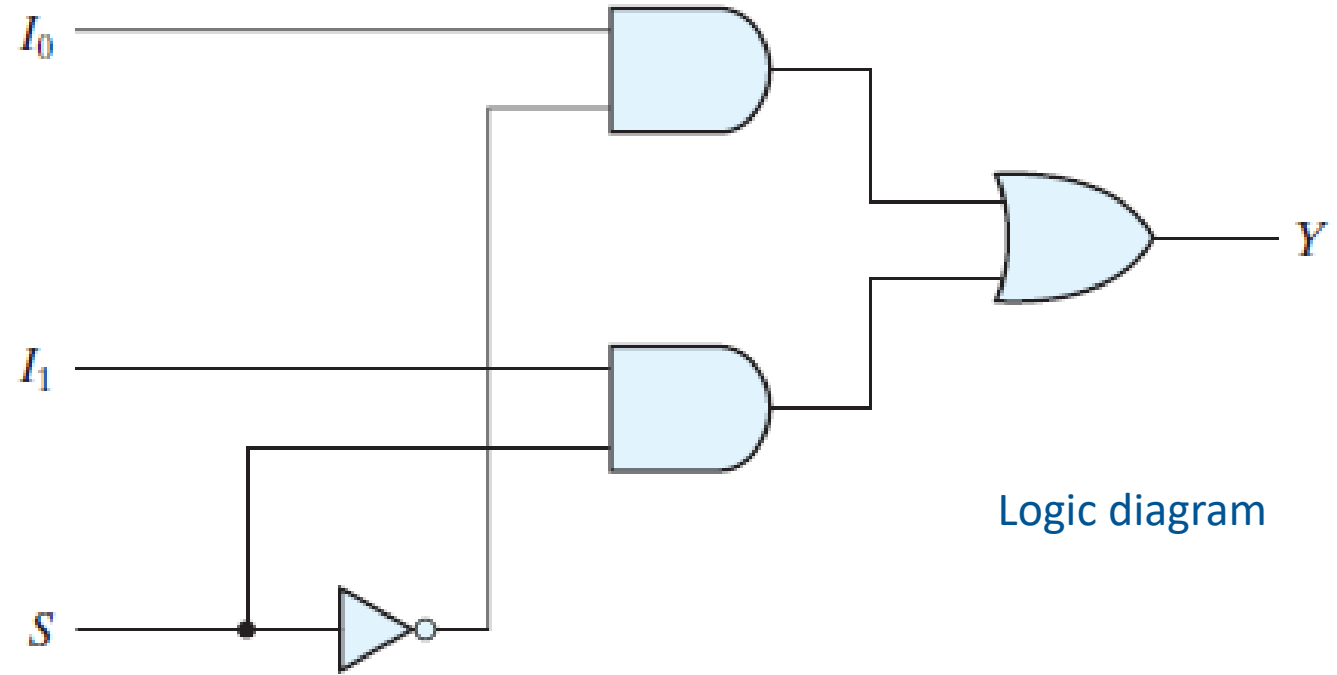
# 2-to-1 mux

- A two-to-one-line multiplexer connects one of two 1-bit sources to a common destination.
- The circuit has two data input lines, one output line, and one selection line  $S$ .
- When  $S = 0$ , upper AND gate is enabled and  $I_0$  has a path to output.
- When  $S = 1$ , lower AND gate is enabled and  $I_1$  has a path to output.




Logic diagram

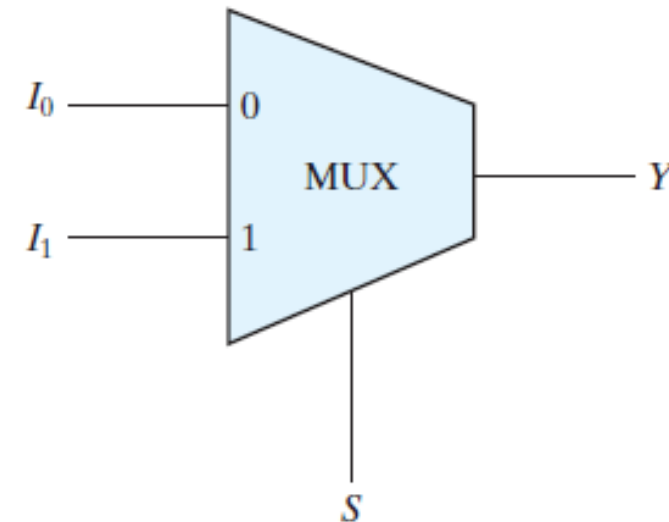



Block diagram
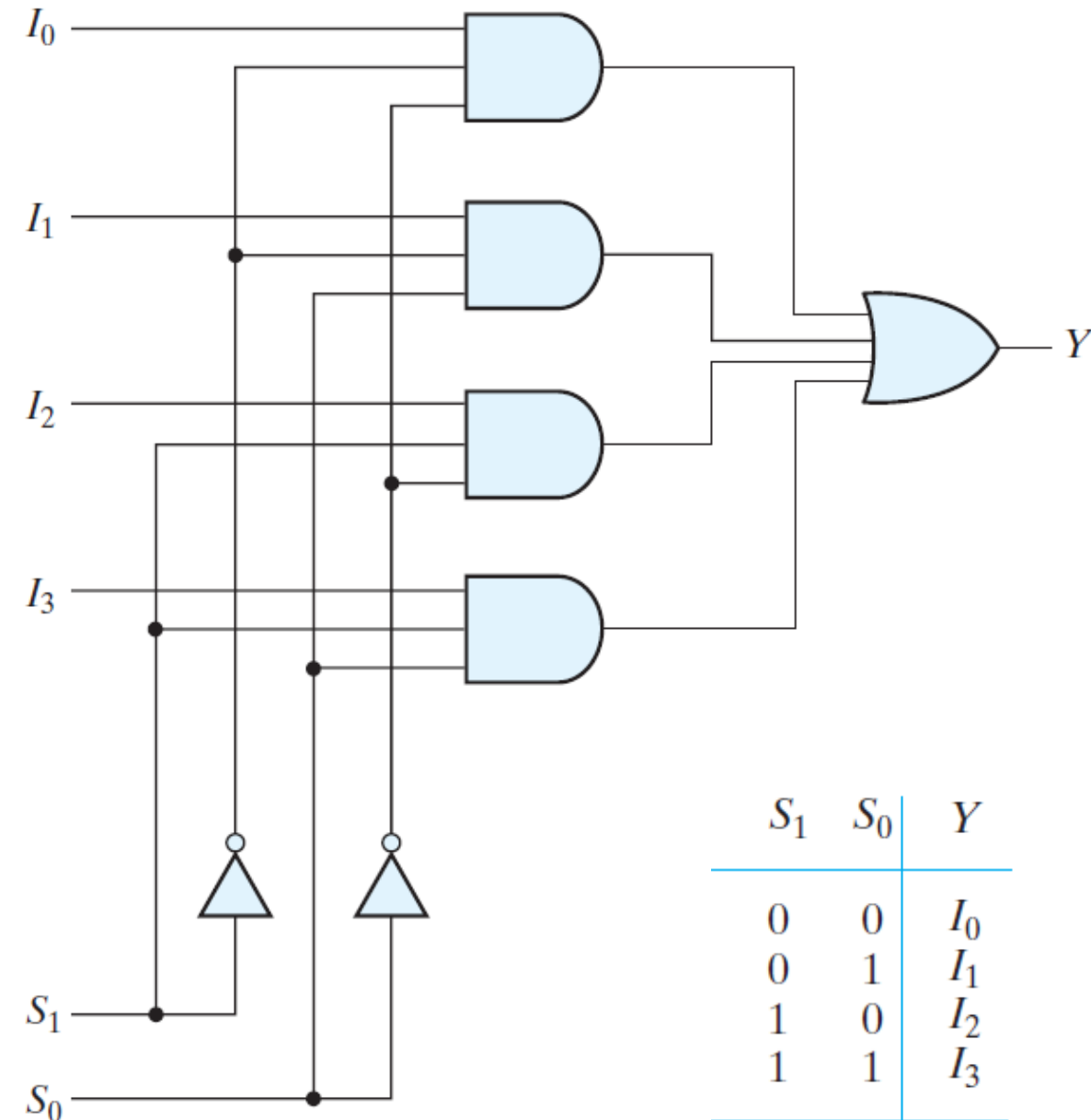
# 4-to-1 mux

- Each of the four inputs,  $I_0$  through  $I_3$ , is applied to one input of an AND gate.
- Selection lines  $S_1$  and  $S_0$  are decoded to select a particular AND gate.
- The outputs of the AND gates are applied to a single OR gate that provides the one-line output.
- MUX is also called a data selector.



# Hierarchical design of MUX

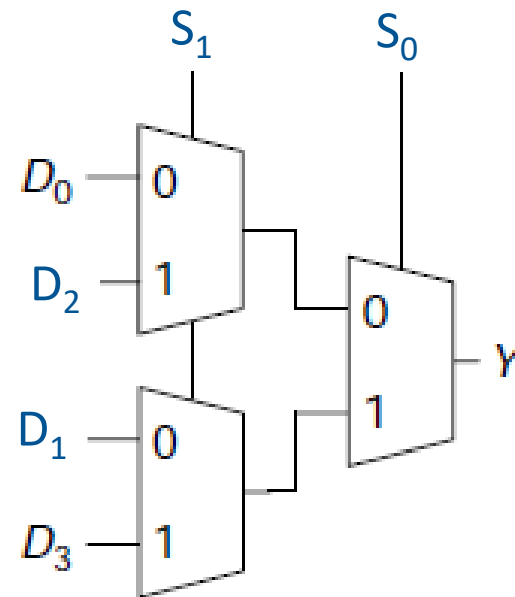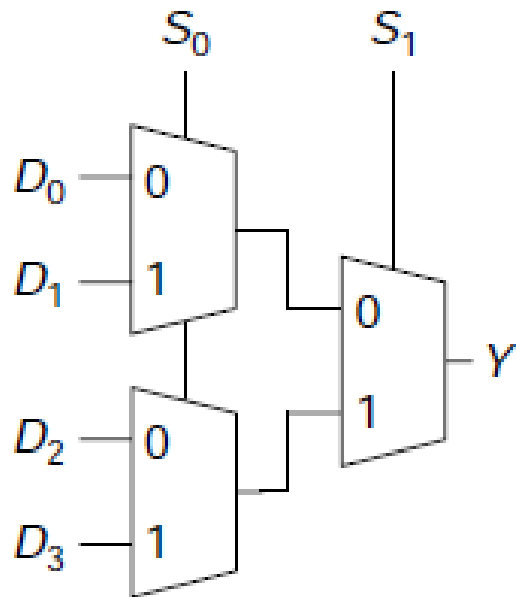

# Connection between mux and decoder

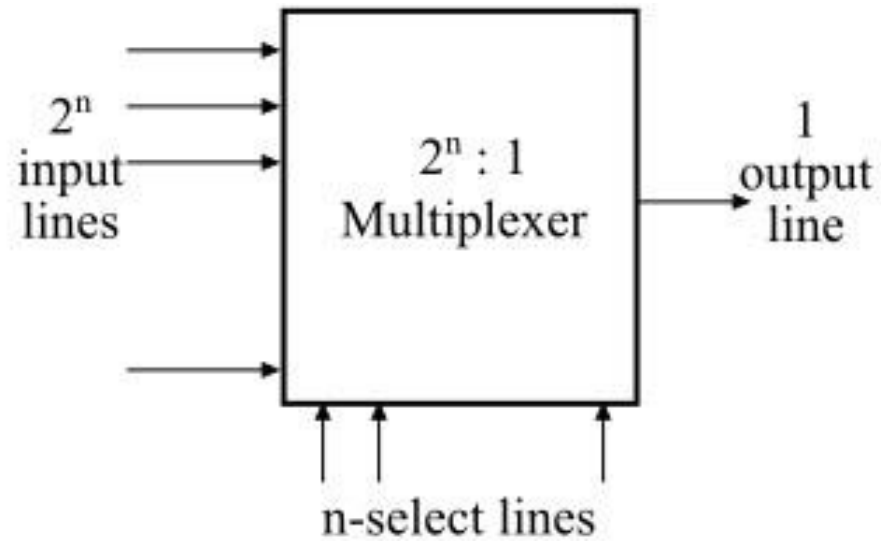


Figure 1 - Multiplexer


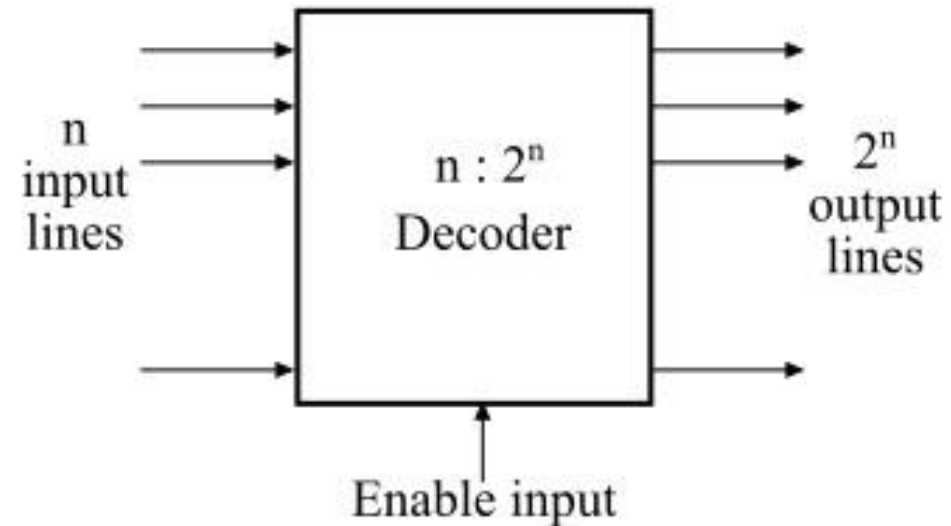


Figure 2 - Decoder

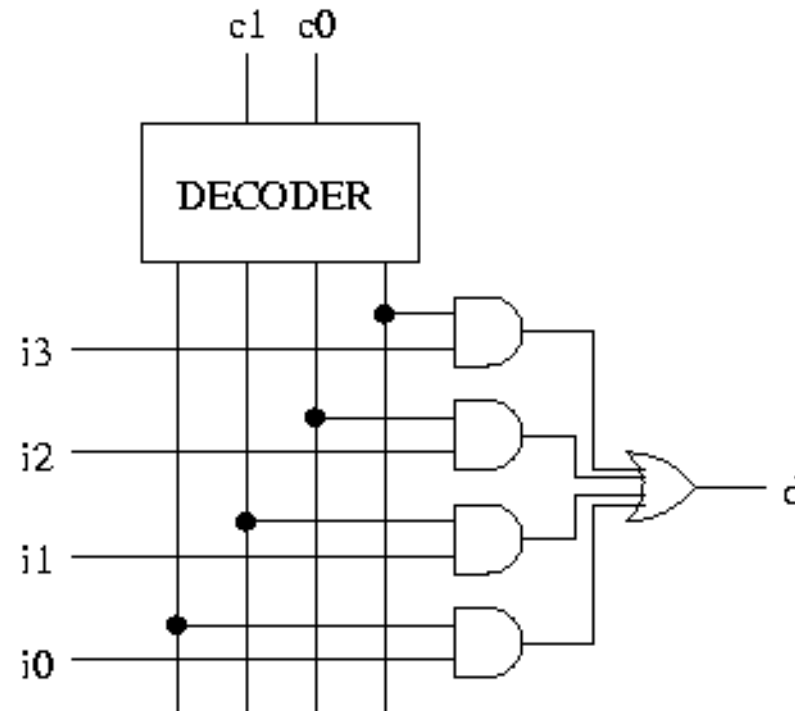
# Designing mux using a decoder

- A  $2^n$ -to-1-line multiplexer is constructed from an  $n$ -to- $2^n$  decoder by adding  $2^n$  input lines to it, one to each AND gate.
- The outputs of the AND gates are applied to a single OR gate.


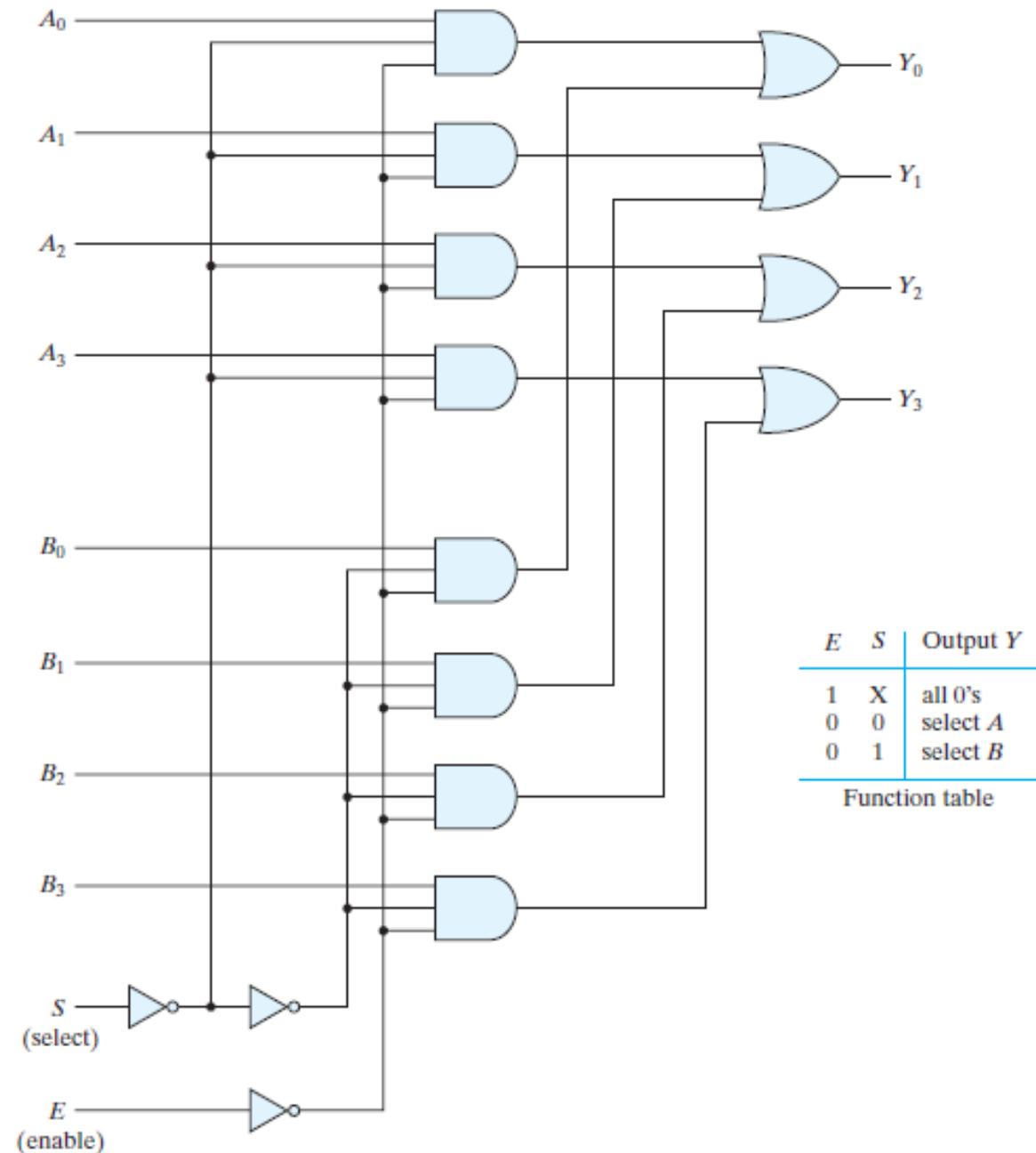
# Multiple-bit selection

- Common selection inputs can be used to provide multiple-bit selection logic.
- This circuit has four MUXes, each capable of selecting one of two input lines.
- Output  $Y_0$  can be selected to come from either input  $A_0$  or input  $B_0$  and so on.
- Input selection line  $S$  selects one of the lines in each of the four MUXes.
- Circuit is enabled using Enable signal






# MUX for implementing a Boolean function

- A MUX is essentially a decoder that includes the OR gate within the unit.
- Minterms of a function are generated in a MUX by the circuit associated with the selection inputs.
- The individual minterms can be selected by the data inputs
- Thus, we can implement a Boolean function of  $n$  variables using a MUX with  $n$  selection inputs and  $2^n$  data inputs, one for each minterm.
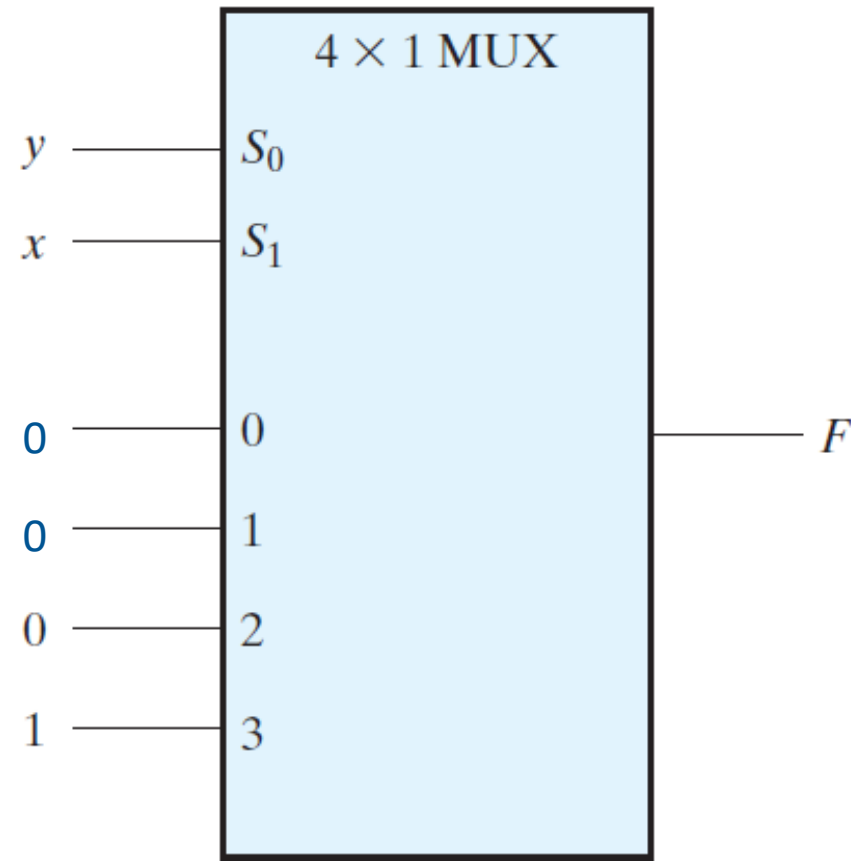
# Implement a 2-input AND function using a 4:1 MUX.



(b) Multiplexer implementation

# More efficient method

- We will implement a Boolean function of  $n$  variables with a MUX that has  $n - 1$  selection inputs.
- The first  $n - 1$  variables of the function are connected to the selection inputs of the multiplexer.
- The remaining single variable of the function is used for the data inputs.
- If the single variable is denoted by  $z$ , each data input of the multiplexer will be  $z$ ,  $z'$ , 1, or 0.

# Implement a 2-input AND function using a 2:1 MUX.


- Inputs are A and B.

A	B	Y=A.B
0	0	0
0	1	0
1	0	0
1	1	1

Y=0

---

Y=B

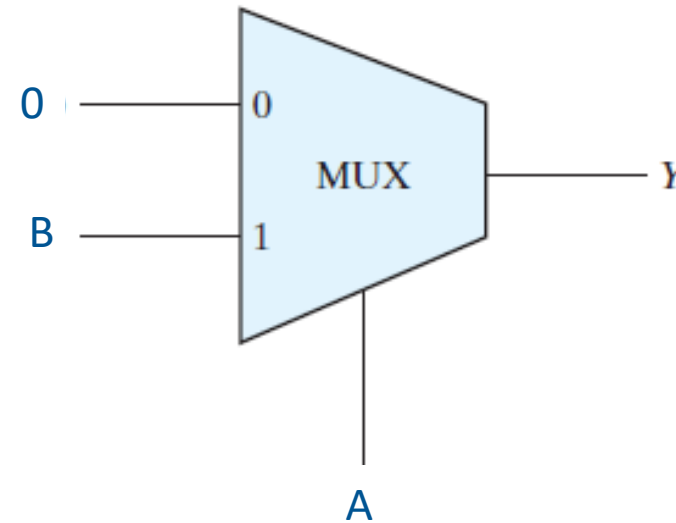


# Example 1

- $F(x, y, z) = \sum(1, 2, 6, 7)$

$x$	$y$	$z$	$F$	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

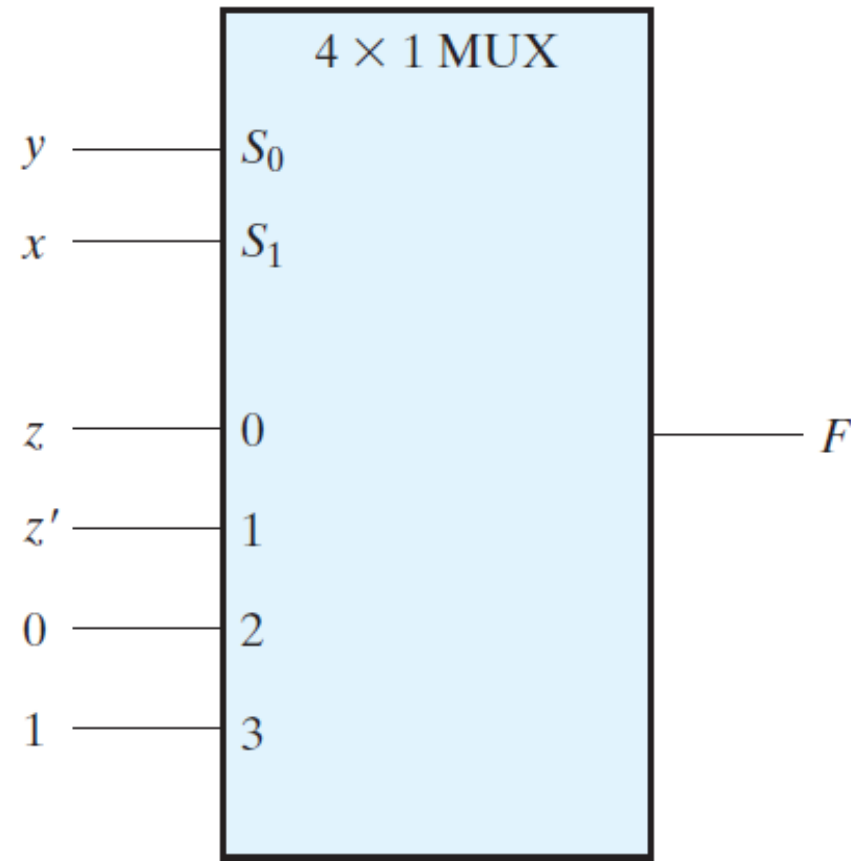

(b) Multiplexer implementation

# Procedure


- Boolean function is listed in a truth table.
- Then first  $n - 1$  variables in the table are applied to the selection inputs of the multiplexer.
- For each combination of the selection variables, we evaluate the output as a function of the last variable.
- This function can be 0, 1, the variable, or the complement of the variable.
- These values are then applied to the data inputs in the proper order.

## Example 2

- $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$
- Variable  $A$  must be connected to selection input  $S2$  so that  $A$ ,  $B$ , and  $C$  correspond to selection inputs  $S2$ ,  $S1$ , and  $S0$ , respectively

$A$	$B$	$C$	$D$	$F$	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

$A$	$B$	$C$	$D$	$F$	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

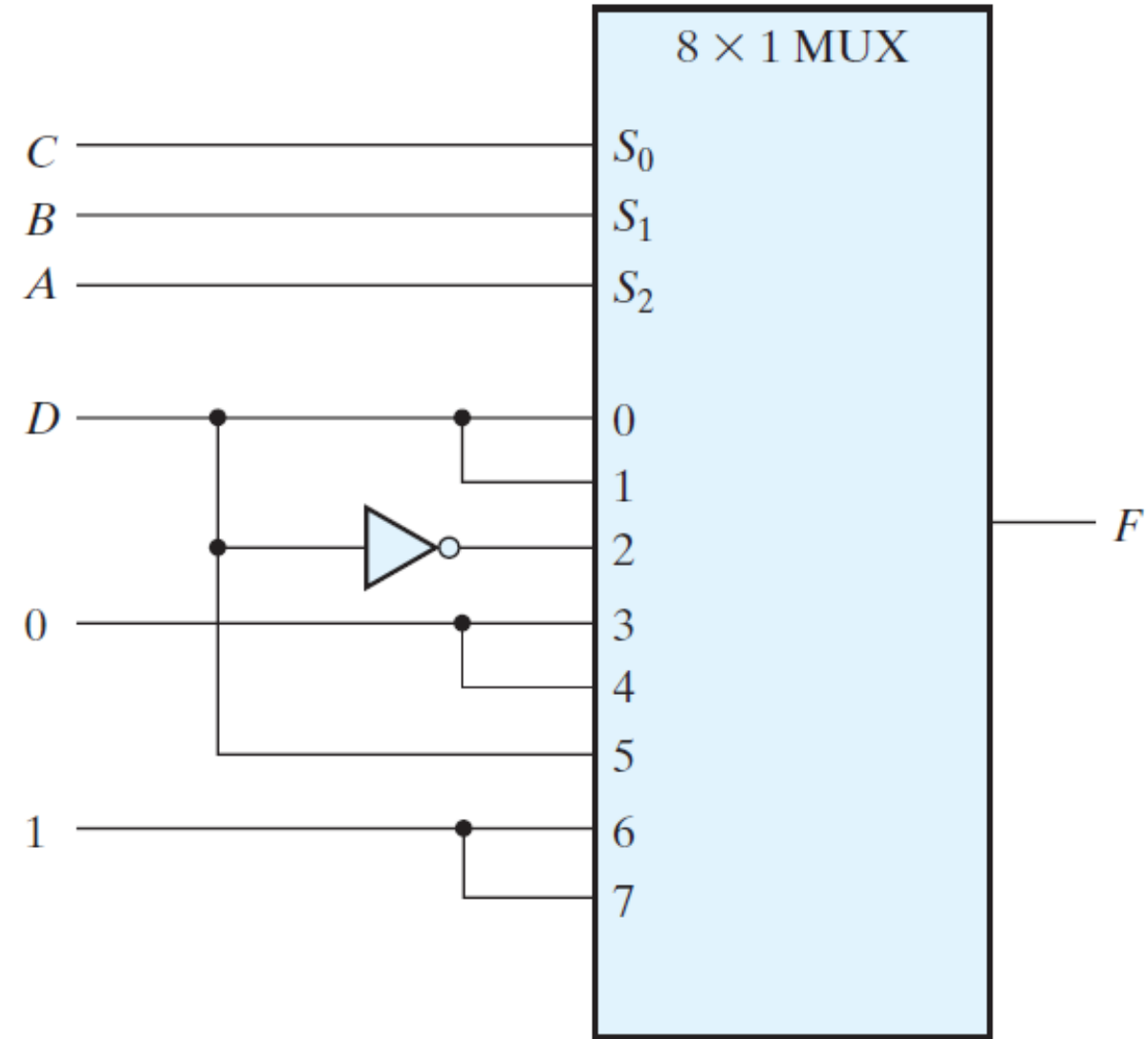



# Application of MUX and DEMUX

- We can design serial data trans-receiver.
- It transmits data bit-by-bit serially.

