 


# Analyzing and Optimizing Combinational Logic Circuit

Sparsh Mittal

# Combinational circuits

- Logic circuits for digital systems may be combinational or sequential.
- A combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs.
- A combinational circuit performs an operation that can be specified logically by a set of Boolean functions.



**FIGURE 4.1**

Block diagram of combinational circuit

# Sequential circuits


- Sequential circuits employ storage elements in addition to logic gates.
- Their outputs are a function of the inputs and the state of the storage elements.
- Because the state of the storage elements is a function of previous inputs, the outputs of a sequential circuit depend not only on present values of inputs, but also on past inputs, and the circuit behavior must be specified by a time sequence of inputs and internal states.

# Combinational circuit

- A combinational circuit can be specified with a truth table that lists the output values for each combination of input variables.
- A combinational circuit also can be described by  $m$  Boolean functions, one for each output variable.
- Each output function is expressed in terms of the  $n$  input variables.
- **The diagram of a combinational circuit has logic gates with no feedback paths or memory elements.**
- A feedback path is a connection from the output of one gate to the input of a second gate whose output forms part of the input to the first gate.
- Feedback paths in a digital circuit define a sequential circuit
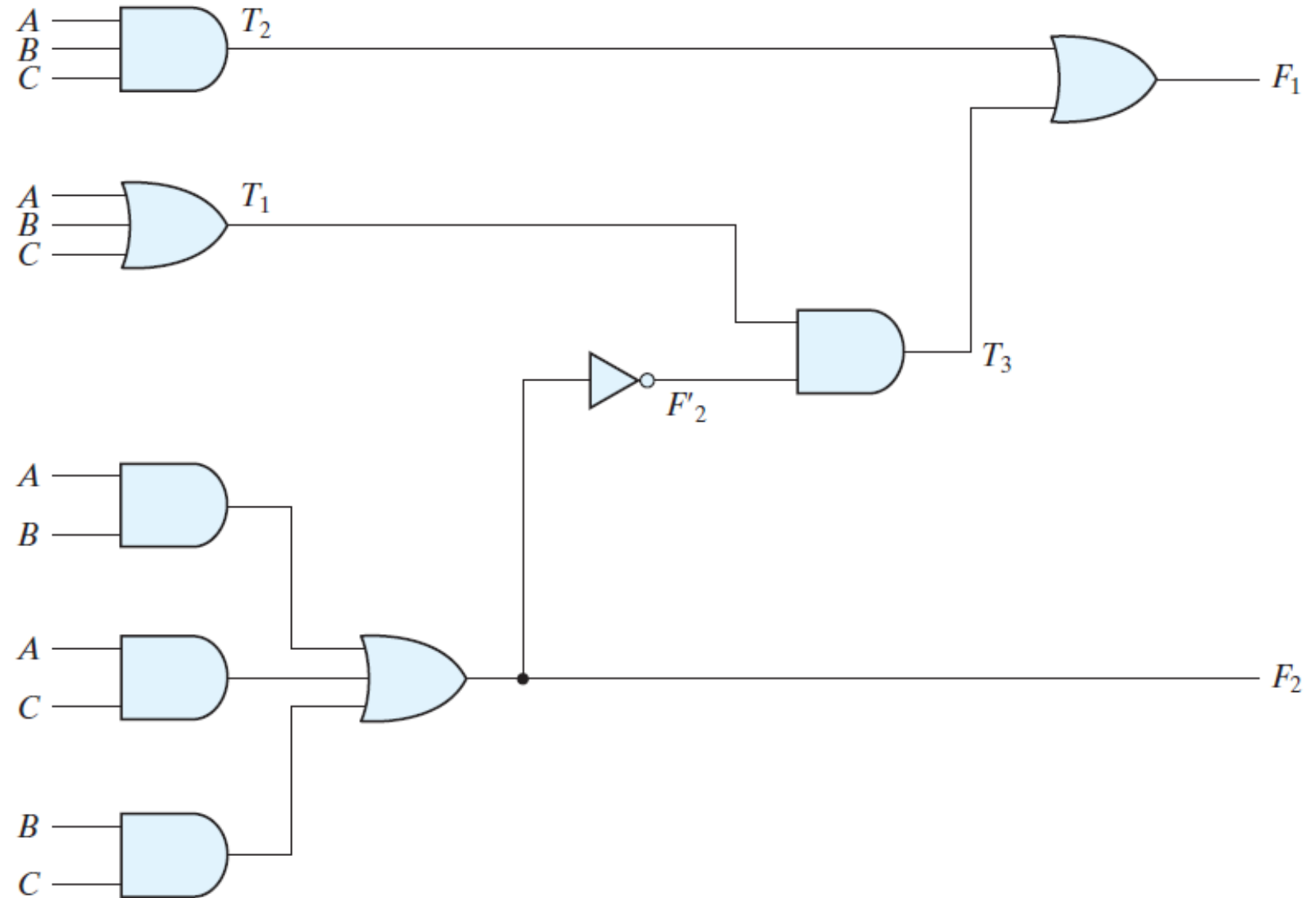
# Example: analyzing a circuit

- Express  $F_1$  and  $F_2$  as function of  $A$ ,  $B$  and  $C$



$$F_2 = AB + AC + BC$$


$$T_1 = A + B + C$$

$$T_2 = ABC$$

$$T_3 = F'_2 T_1$$

$$F_1 = T_3 + T_2$$
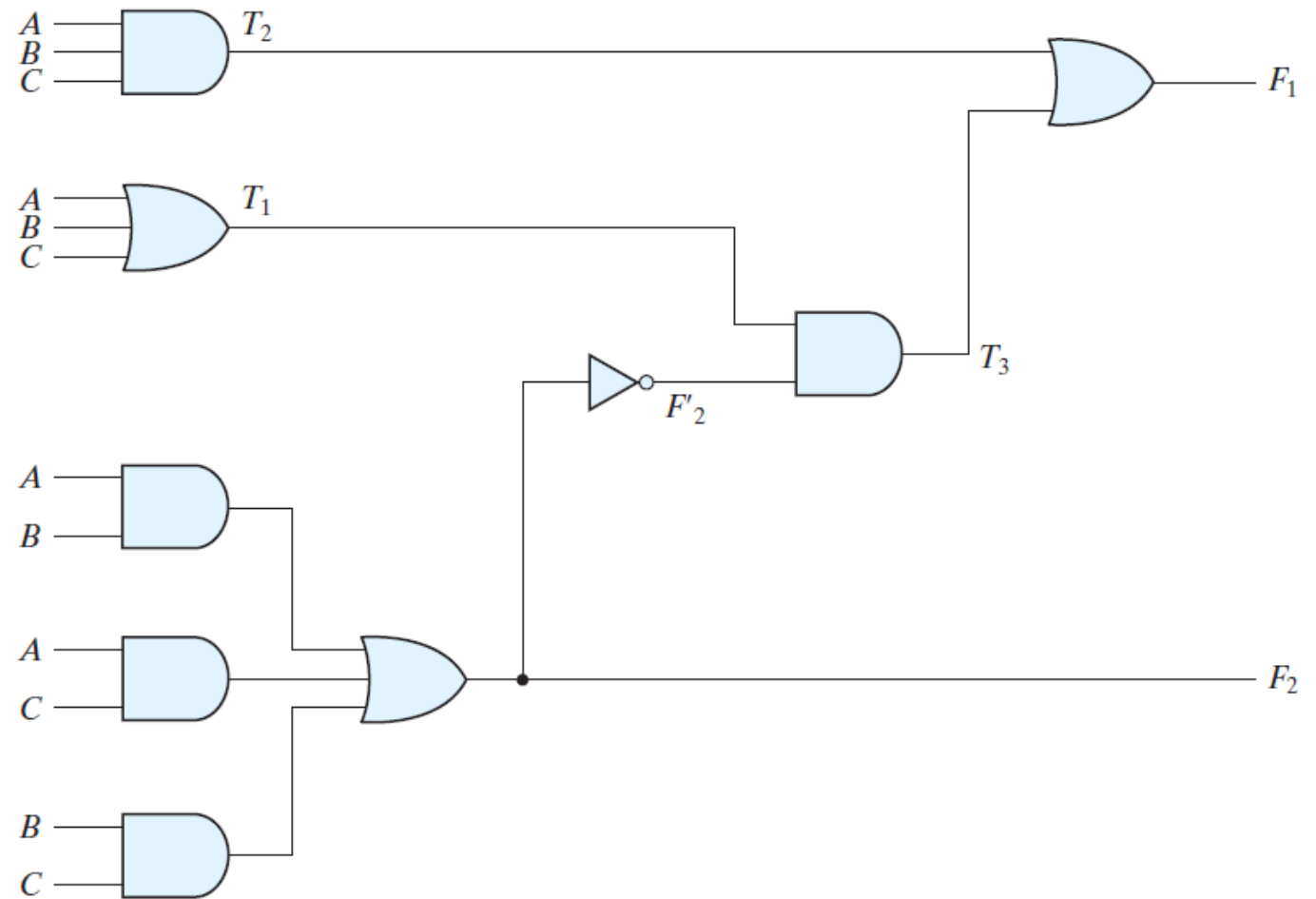
$$\begin{aligned} F_1 &= T_3 + T_2 = F'_2 T_1 + ABC = (AB + AC + BC)'(A + B + C) + ABC \\ &= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\ &= (A' + B'C')(AB' + AC' + BC' + B'C) + ABC \\ &= A'BC' + A'B'C + AB'C' + ABC \end{aligned}$$



# Determining truth table

*Truth Table for the Logic Diagram of Fig. 4.2*

<b><i>A</i></b>	<b><i>B</i></b>	<b><i>C</i></b>	<b><i>F</i><sub>2</sub></b>	<b><i>F</i>'<sub>2</sub></b>	<b><i>T</i><sub>1</sub></b>	<b><i>T</i><sub>2</sub></b>	<b><i>T</i><sub>3</sub></b>	<b><i>F</i><sub>1</sub></b>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Inspection of the truth table combinations for  $A$ ,  $B$ ,  $C$ ,  $F_1$ , and  $F_2$  shows that it is identical to the truth table of the full adder given in Section 4.5 for  $x$ ,  $y$ ,  $z$ ,  $S$ , and  $C$ , respectively.

# Code conversion example

- Converts binary coded decimal (BCD) to the excess-3 code for the decimal digits.

<i>Decimal</i>	<i>BCD</i>	<i>Excess-3</i>
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100



# BCD to Excess-3 conversion

*Truth Table for Code Conversion Example*

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

- We designate the four input binary variables by symbols *A*, *B*, *C*, and *D*, and four output variables by *w*, *x*, *y*, and *z*.
- Four binary variables may have 16 bit combinations, but only 10 are listed in the truth table.
- The six input bit-combinations not listed for the input variables are don't-care combinations.
- We assume that they will never occur.
- Therefore, we are at liberty to assign to the output variables either a 1 or a 0, whichever gives a simpler circuit.

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X
		D			

$z = D'$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$	$m_{11}$ X	$m_{10}$ X
		D			

$y = CD + C'D'$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$ 1	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$	$m_9$ 1	$m_{11}$ X	$m_{10}$ X
		D			

$x = B'C + B'D + BC'D'$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ X
		D			

$w = A + BC + BD$

# Further optimization


- The expressions obtained may be manipulated algebraically for using common gates for two or more outputs.
- This manipulation illustrates the flexibility obtained with multiple-output systems when implemented with three or more levels of gates:

$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$\begin{aligned} x &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)' \end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$

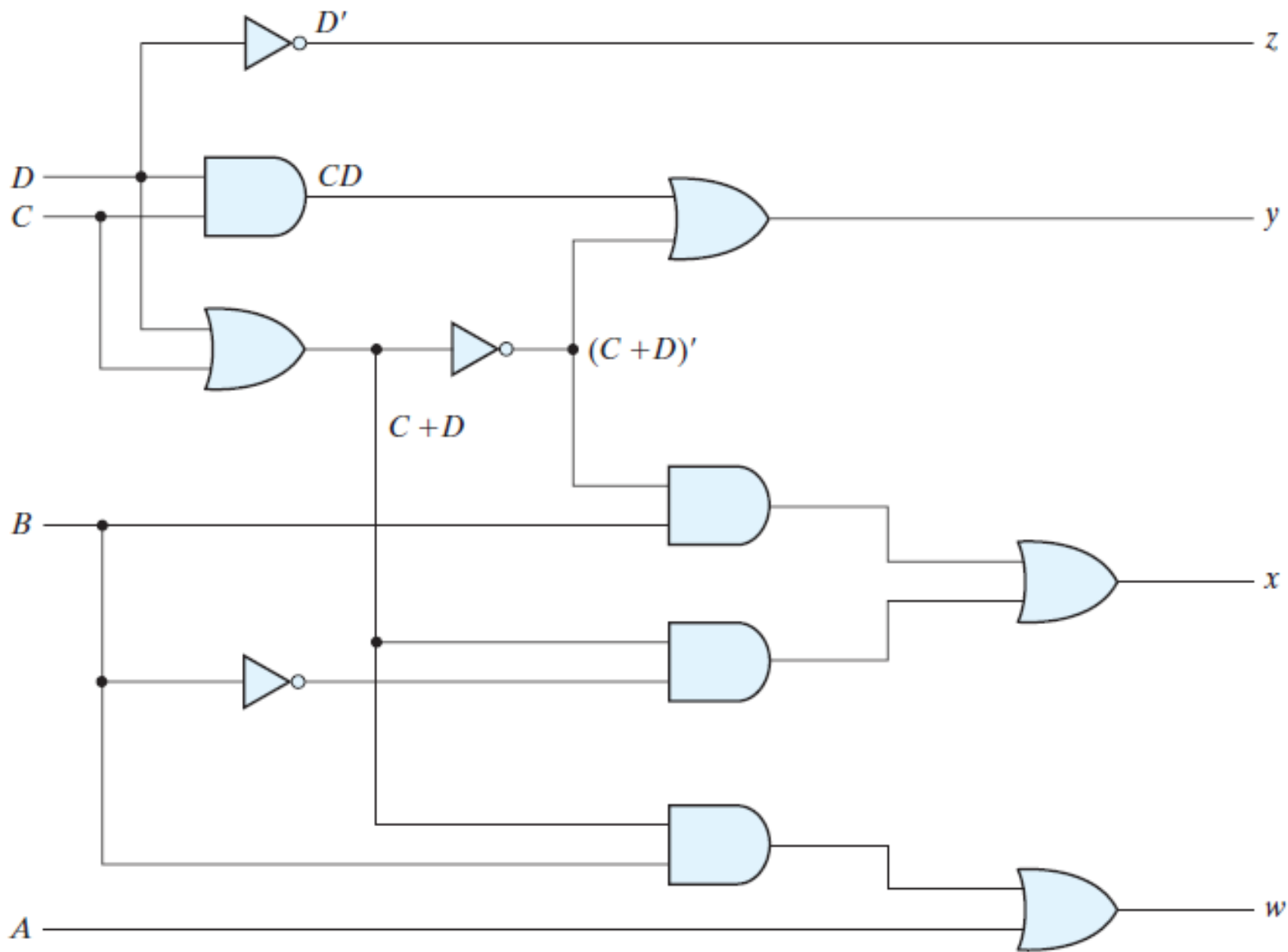

Three-level logic circuit requires fewer gates, all of which in turn require no more than two inputs

**FIGURE 4.4**

Logic diagram for BCD-to-excess-3 code converter