

Ripple (Asynchronous) Counters

Sparsh Mittal



What is a counter?

A register that goes through a prescribed sequence of states upon the application of input pulses is called a *counter*

A counter that follows the binary number sequence is called a *binary counter*.

An n -bit binary counter consists of n flip-flops and can count in binary from 0 through $2^n - 1$.


Ripple vs synchronous counters

Two types of counters: ripple (asynchronous) and synchronous.


Ripple: a flip-flop output transition serves as a source for triggering other flip-flops.

In other words: C input of some or all flip-flops are triggered, not by the common clock pulses, but rather by the transition that occurs in other flip-flop outputs.

 Synchronous: C inputs of all flip-flops receive the common clock.



Ripple (asynchronous)

 

Synchronous

Background: How to design complementing flip-flop

1. From a JK flip-flop with the J and K inputs tied together to 1
2. From a T flip-flop (with $T=1$).
3. Use a D flip-flop with the complement output connected to the D input. In this way, the D input is always the complement of the present state, and the next clock pulse will cause the flip-flop to complement.



Asynchronous (ripple) counter

Binary ripple counter

It has a series connection of complementing flip-flops, with the output of each flip-flop connected to the C input of the next higher order flip-flop.

The flip-flop holding the least significant bit receives the incoming count pulses.

Lets observe the pattern of bit-flips

Pattern of flips

A0 is complemented with each count pulse input.

Every time A0 goes from 1 to 0, it complements A1.

Every time that A1 goes from 1 to 0, it complements A2.

Every time that A2 goes from 1 to 0, it complements A3.

Based on this observation, we design the circuit.

Binary Count Sequence (0 to 8)

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

Circular counting from 0 → 15 → 0

Four-bit binary ripple counter

D Flip-Flop


D	$Q(t + 1)$
0	0 Reset
1	1 Set

T Flip-Flop

T	$Q(t + 1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

Output of each flip-flop is connected to the C input of the next flip-flop.

 In (a), Each flip-flop complements if the signal in its C input goes through a negative transition (negative edge triggered, i.e., when output of previous flip-flop goes from 1 to 0).



Signal propagation in ripple fashion

Consider transition from 0011 to 0100. A0 is complemented with the count pulse.

Since A0 goes from 1 to 0, it triggers A1 and complements it.

As a result, A1 goes from 1 to 0, which in turn complements A2, changing it from 0 to 1.

A2 does not trigger A3, because A2 produces a positive transition and the flip-flop responds only to negative transitions.

Thus, the count from 0011 to 0100 is achieved by changing the bits one at a time.

Binary countdown counter

Counts from 15 to 0.

LSB is complemented with every count pulse.


Any other bit is complemented if its previous LSB goes from 0 to 1.

Therefore, a countdown counter looks the same as the binary ripple counter shown earlier, except that all flip-flops trigger on the positive clock-edge. (Bubble in the C inputs must be absent.)

Multiplexers for Parallel-to-Serial Data Conversion

Although data are processed in parallel in many digital systems to achieve faster processing speeds, when it comes to transmitting these data relatively large distances, this is done serially.

Application of asynchronous counter

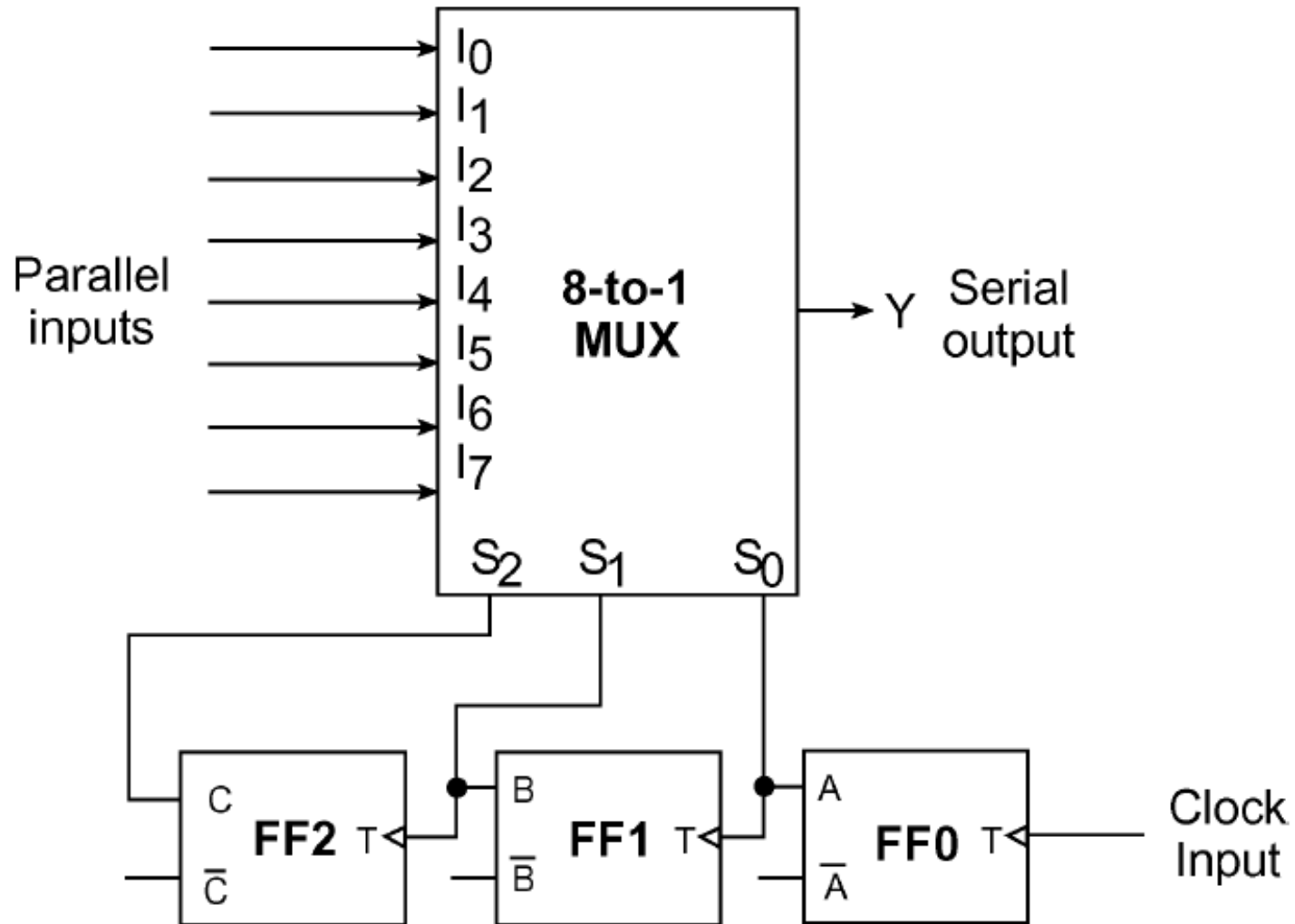


- An 8-to-1 multiplexer is used to convert eight-bit parallel binary data to serial form.
- A three-bit counter controls the selection inputs.
- As the counter goes through 000 to 111, the multiplexer output goes through I₀ to I₇.
- The conversion process takes a total of eight clock cycles.
- Here, we have used 3 T flip-flops.



BCD Ripple Counter

BCD Ripple Counter

 A decimal counter is similar to a binary counter, except that the state after 1001_2 (9) is 0000_2 (0).



Counting sequence

Q1 changes state after each clock pulse.

Q2 complements every time **Q1** goes from 1 to 0, as long as **Q8** = 0.

When **Q8** becomes 1, **Q2** remains at 0.

Q4 complements every time **Q2** goes from 1 to 0.

Q8 remains at 0 as long as **Q2** or **Q4** is 0.

When both **Q2** and **Q4** become 1, **Q8** complements when **Q1** goes from 1 to 0.

Q8 is cleared on the next transition of **Q1**.

Clock	Counter Output				State Number	BCD Number
	Q8	Q4	Q2	Q1		
Initially	0	0	0	0	—	0000
1 st	0	0	0	1	1	0001
2 nd	0	0	1	0	2	0010
3 rd	0	0	1	1	3	0011
4 th	0	1	0	0	4	0100
5 th	0	1	0	1	5	0101
6 th	0	1	1	0	6	0110
7 th	0	1	1	1	7	0111
8 th	1	0	0	0	8	1000
9 th	1	0	0	1	9	1001
10 th	0	0	0	0	0	0000

BCD Ripple Counter


Table 5.1
Flip-Flop Characteristic Tables

JK Flip-Flop			
J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

Output of Q_1 is applied to the C inputs of both Q_2 and Q_8 and output of Q_2 is applied to the C input of Q_4 .

The J and K inputs are connected either to a permanent 1 signal or to outputs of other flip-flops.

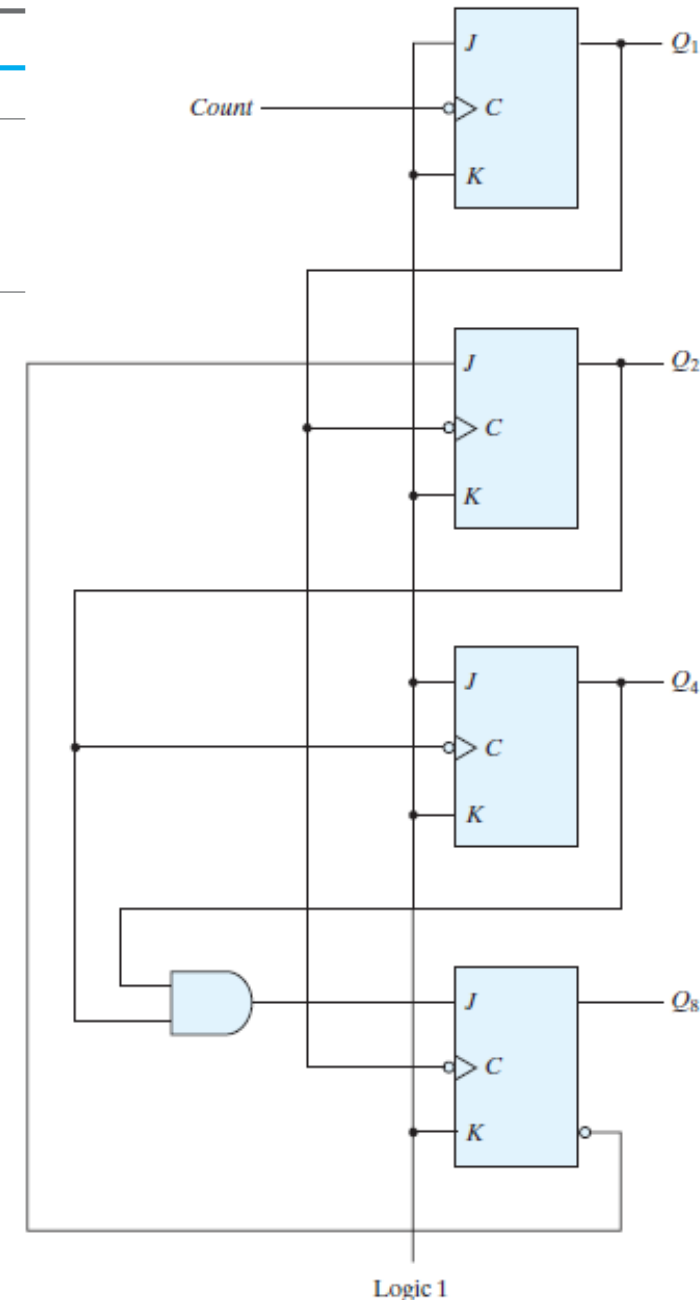Remember that when the C input goes from 1 to 0, flip-flop is set if $J = 1$, is cleared if $K = 1$, is complemented if $J = K = 1$, and is left unchanged if $J = K = 0$.



BCD Ripple Counter

Table 5.1

Flip-Flop Characteristic Tables

<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q'(t)</i>	Complement

Q1 changes state after each clock pulse.

Q2 complements every time **Q1** goes from 1 to 0, as long as $Q8 = 0$.


When Q_8 becomes 1, Q_2 remains at 0.

Q4 complements every time **Q2** goes from 1 to 0.

Q_8 remains at 0 as long as Q_2 or Q_4 is 0.

When both $Q2$ and $Q4$ become 1, $Q8$ complements when $Q1$ goes from 1 to 0.

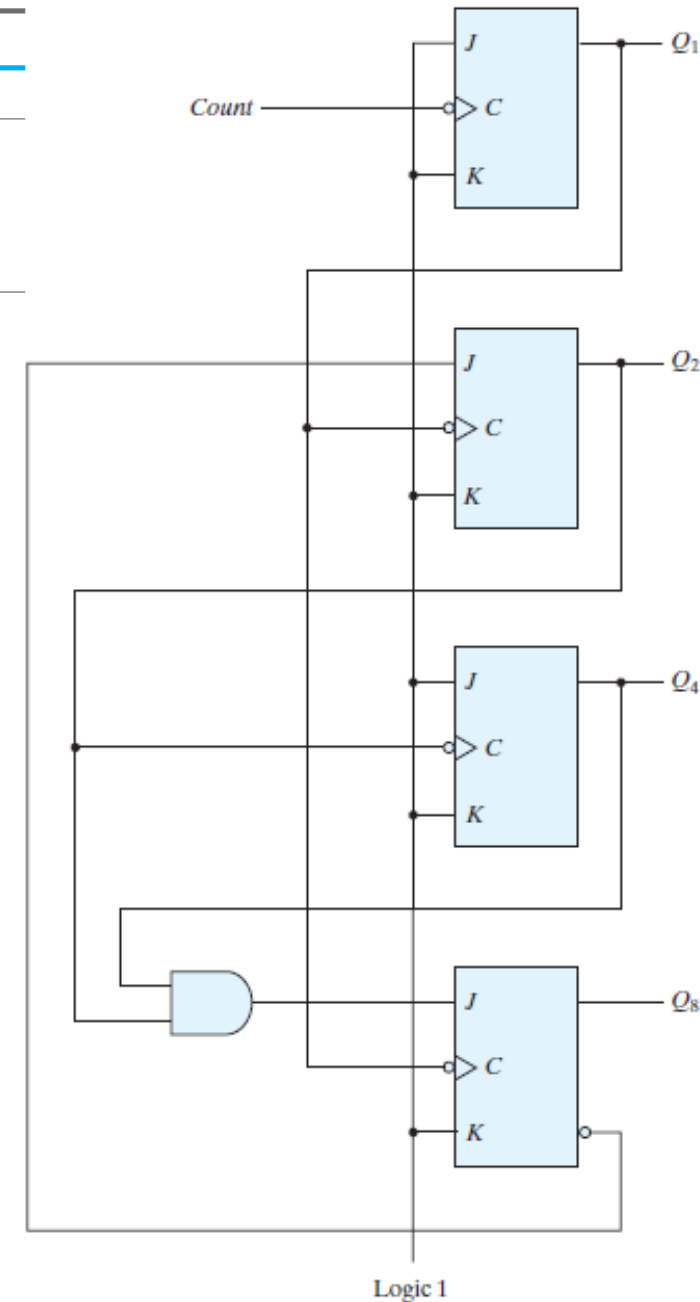$Q8$ is cleared on the next transition of $Q1$.




Multi-decade counter

BCD counter shown previously was a decade counter (counts from 0 to 9).

To count from 0 to 999, we need a three-decade counter.

The inputs to second and third decades come from Q_8 of previous decade.

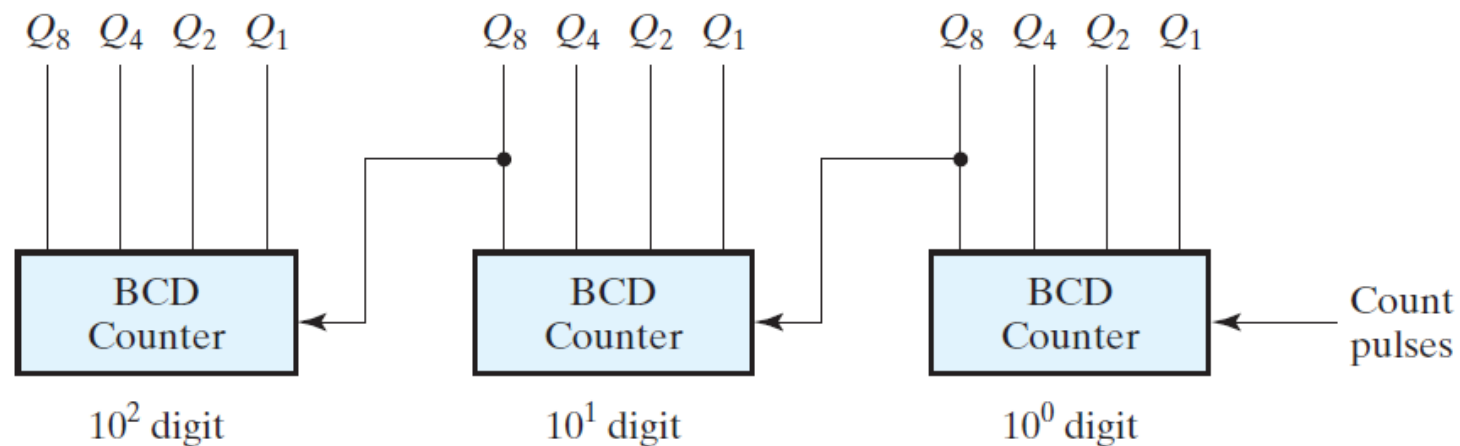When Q_8 in one decade goes from 1 to 0, it triggers the count for the next higher order decade while its own decade goes from 9 to 0.



Block diagram of a three-decade decimal BCD counter

Mod-N counter


Modulus *Counters*, or simply *MOD counters*, are defined by the number of states they will cycle through before returning to their original value.

A decade *counter* is called as *mod -10* or divide by 10 *counter*. It counts from 0 to 9 and again reset to 0

Mod-3 counter using 3 flip-flops

A 3-bit binary counter will work as MOD-3 counter if A_1 and A_0 are NANDed and output of NAND gate is ANDed with reset.

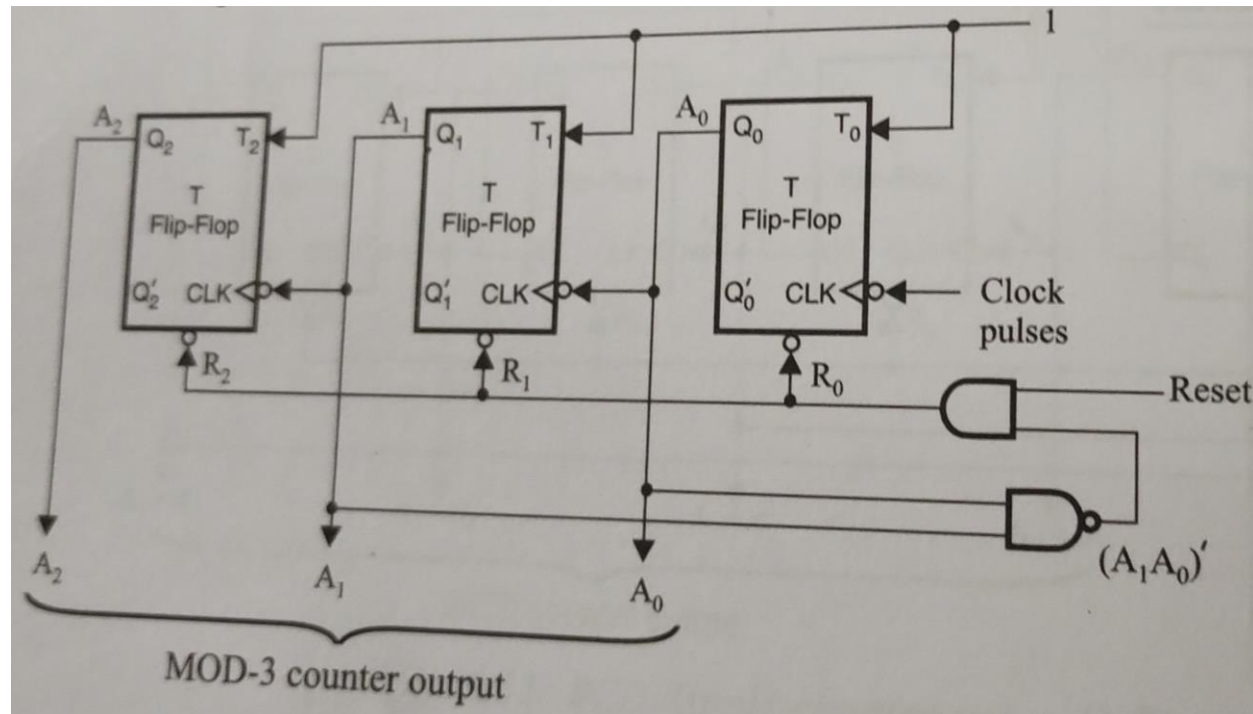Now, the counter will reset in every third clock pulse.



Clock pulse	A_2	A_1	A_0
1	0	0	0
2	0	0	1
3	0	1	0

Limitation of asynchronous counter

They suffer from “Propagation Delay” in which the timing signal is delayed by a fraction through each flip-flop.

In **synchronous counter**, the external clock signal is connected to the clock input of EVERY individual flip-flop within the counter so that all of the flip-flops are clocked together simultaneously at the same time giving a fixed time relationship.

==> Changes in the output occur in “synchronisation” with the clock signal.

==> no ripple effect and no propagation delay.

==> The maximum operating frequency of this counter is much higher than that for a similar asynchronous counter.